

Problem Set 4 — RC Circuit Transient Analysis

1. A series RC circuit has $R = 10 \text{ k}\Omega$ and $C = 47 \text{ }\mu\text{F}$, connected to a 12V DC source at $t = 0$. Derive the expression for the voltage across the capacitor $V_C(t)$ during charging.
2. For the circuit in Problem 1, calculate:
 - (a) The time constant τ
 - (b) The voltage across the capacitor at $t = 2\tau$
 - (c) The time required for the capacitor to reach 99% of its final voltage
3. Find the total energy stored in the capacitor at steady state and compare it to the total energy delivered by the source.
4. Sketch $V_C(t)$ and $I(t)$ curves for both the charging phase ($0 \leq t \leq 5\tau$) and the discharging phase. Label key values on each axis.
5. A capacitor initially charged to 12V is connected at $t = 0$ to a network of two resistors: $R_1 = 4 \text{ k}\Omega$ in series with the parallel combination of $R_2 = 6 \text{ k}\Omega$ and $R_3 = 3 \text{ k}\Omega$. Find the current through R_2 immediately after the switch closes, and find the time constant of the discharge.

1) KVL around the loop gives $V_s = V_R + V_C$ so

$$V_s = RC \frac{dV_C}{dt} + V_C$$

This is a first order ODE with $V_C(0) = 0$, rearrange and separate:

$$\frac{dV_C}{V_s - V_C} = \frac{dt}{RC}$$

Integrating both sides: $-\ln(V_s - V_C) = t/RC + \text{const}$. Using $V_C(0) = 0$ gives $\text{const} = -\ln V_s$ so

$$V_C(t) = V_s(1 - e^{-t/RC}) = 12(1 - e^{-t/0.17}) \text{ V}$$

where t is in seconds

2a) The time constant is

$$\tau = RC = (10 \times 10^6)(17 \times 10^{-6}) = 0.17 \text{ s}$$

2b) At $t = \tau$:

$$V_C(\tau) = 12(1 - e^{-1}) = 12 - 0.35 = 11.65 \text{ V} \approx 11.7 \text{ V}$$

2c) We need $V_C = 0.99 \times 12$ so $1 - e^{-t/\tau} = 0.99$ which gives $e^{-t/\tau} = 0.01$. Then

$$t = -\tau \ln(0.01) = 0.17 \times 4.605 \approx 0.78 \text{ s} \approx 0.8 \text{ s}$$

3) Energy stored in the capacitor at steady state ($V_C = 12 \text{ V}$):

$$E_C = \frac{1}{2} C V_s^2 = \frac{1}{2} (10 \times 10^{-6})(12)^2 = 7.2 \times 10^{-4} \text{ J} \approx 0.72 \text{ mJ}$$

The total charge delivered by the source is $Q = CV_s$ so the total energy from the source is


$$E_s = QV_s = CV_s^2 = (10 \times 10^{-6})(144) = 1.44 \text{ mJ}$$

So the capacitor stores exactly half the energy delivered by the source. The other half 0.72 mJ is dissipated as heat in the resistor. This 50/50 split holds regardless of R .

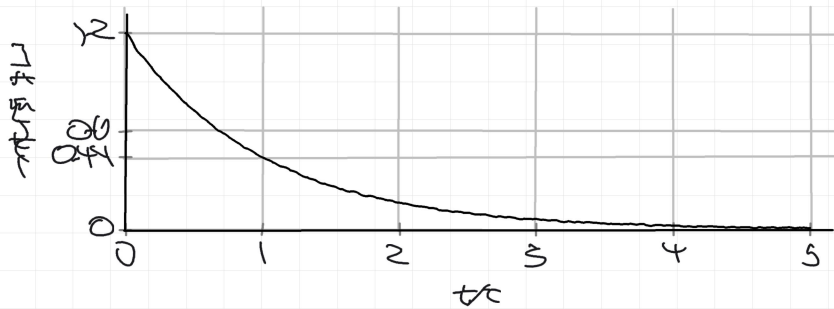4)


Charging phase ($0 \leq t \leq 5\tau$): $V_C(t) = 12(1 - e^{-t/\tau})$ and $i(t) = \frac{12}{RC} e^{-t/\tau} = 12e^{-t/\tau} \text{ mA}$





Key values during charging: at $t=0$, $V_C = 0$ V and $I = 1.2$ mA. At $t = \tau$, $V_C \approx 738$ V and $I \approx 0.4$ mA. At $t = 5\tau$, $V_C \approx 1.92$ V and $I \approx 0.038$ mA (essentially zero).

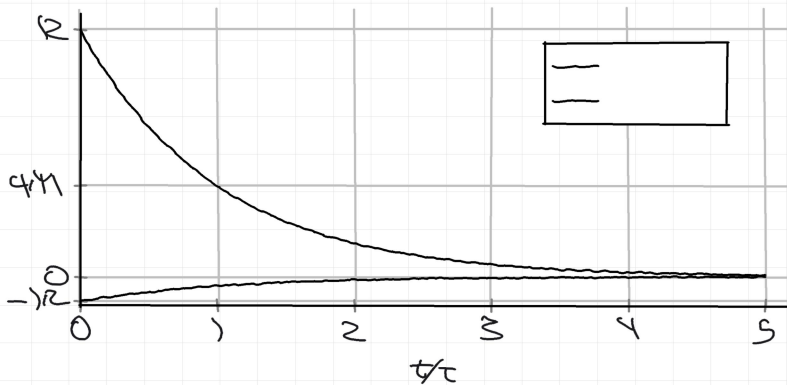Discharging phase: capacitor starts at 2V and decays through R. Now $V_C(t) = 2e^{-t/\tau}$ and $I(t) = -1.2e^{-t/\tau}$ mA (current reverses direction).



At $t = \tau$, $V_C \approx 4/11$ V. At $t = 5\tau$, $V_C \approx 738$ V (essentially discharged).

3) First find the equivalent resistance seen by the capacitor. R_2 and R_3 are in parallel:

$$R_{23} = \frac{R_2 R_3}{R_2 + R_3} = \frac{(6)(3)}{6+3} = 2 \text{ k}\Omega$$

This is in series with R_1 , so the total resistance is

$$R_{eq} = R_1 + R_{23} = 4 + 2 = 6 \text{ k}\Omega$$

At $t=0^+$, the capacitor still has 12V across it so the total current leaving the capacitor is

$$I_{total} = \frac{12}{R_{eq}} = \frac{12}{6000} = 2 \text{ mA}$$

This 2 mA flows through R_1 and then splits between R_2 and R_3 . Using the current divider (current splits inversely with resistance):

$$I_{R2} = I_{total} \times \frac{R_3}{R_2 + R_3} = 2 \times \frac{3}{6+3} = \frac{2}{3} \text{ mA} \approx 0.667 \text{ mA}$$

The discharge time constant is

$$\tau = R_{eq} C = (6 \times 10^3) \times (7 \times 10^{-6}) = 0.042 \text{ s}$$